



**UNIT**

**2**

CURRENT ELECTRICITY

**Dr. Rita John**

**Professor & Head**

**Department of Theoretical Physics**

**University of Madras**

**Chennai**


# Charges

- Charges at rest
- Charges at random motion
- Charges moving in a particular direction  
(drifting of charges)

## 2.1

# ELECTRIC CURRENT

### 2.1.1 Conventional Current

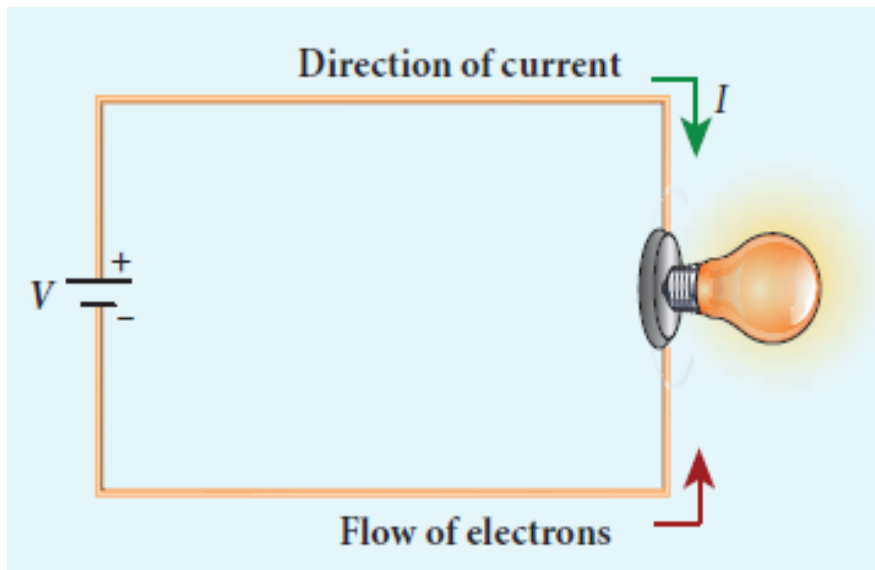

**Figure 2.3** Direction of conventional current and electron flow

If a net charge  $Q$  passes through any cross section of a conductor in time  $t$ , then the current is defined as  $I = \frac{Q}{t}$ . But charge flow is not always constant. Hence current can more generally be defined as

$$I_{avg} = \frac{\Delta Q}{\Delta t} \quad (2.1)$$

Where  $\Delta Q$  is the amount of charge that passes through the conductor at any cross section during the time interval  $\Delta t$ . If the rate at which charge flows changes in time, the current also changes. The instantaneous current  $I$  is defined as the limit of the average current, as  $\Delta t \rightarrow 0$

$$I = \lim_{\Delta t \rightarrow 0} \frac{\Delta Q}{\Delta t} = \frac{dQ}{dt} \quad (2.2)$$

# Current

1. If a net charge  $Q$  passes through any cross section of a conductor in time  $t$ , then the current is defined as  $I = \frac{Q}{t}$

2. Charge flow is not always constant.  
current (more general)

$$I_{avg} = \frac{\Delta Q}{\Delta t}$$

3. If the rate at which charge flows changes in time, the current also changes.

The instantaneous current  $I$  is defined as the limit of the average current, as

$$I = \lim_{\Delta t \rightarrow 0} \frac{\Delta Q}{\Delta t} = \frac{dQ}{dt}$$

## 2.1.2 Drift velocity

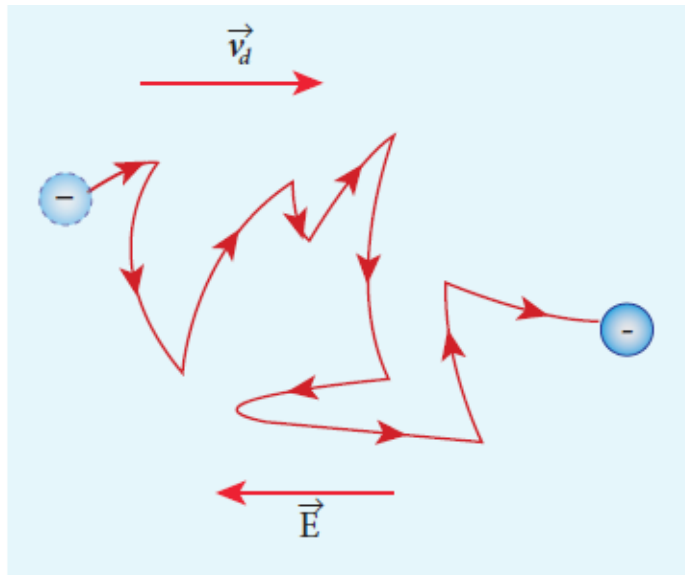


Figure 2.4 Electric current

$$\vec{a} = \frac{-e\vec{E}}{m} \quad (\text{since } \vec{F} = -e\vec{E}) \quad (2.3)$$

The drift velocity  $\vec{v}_d$  is given by

$$\vec{v}_d = \vec{a} \tau$$

$$\vec{v}_d = -\frac{e\tau}{m}\vec{E} \quad (2.4)$$

$$\vec{v}_d = -\mu\vec{E} \quad (2.5)$$

Here  $\mu = \frac{e\tau}{m}$  is the mobility of the electron and it is defined as the magnitude of the drift velocity per unit electric field.

$$\mu = \frac{|\vec{v}_d|}{|\vec{E}|} \quad (2.6)$$

### 2.1.3 Microscopic model of current

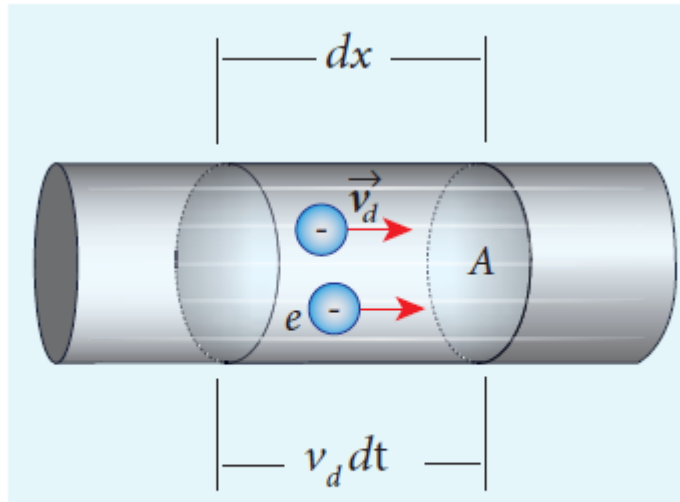


Figure 2.5 Microscopic model of current

Step 1: The electrons available in the volume element

$$= (A v_d dt) n$$

Step 2 : Total charge in volume element

$$dQ = (e)(A v_d dt) n$$

Step 3: Current:

$$\text{current } I = \frac{dQ}{dt} = \frac{neAv_d dt}{dt}$$

$$I = ne A v_d$$

Step 4: Current density J

$$J = \frac{I}{A}$$

Substituting ....

$$\vec{J} = -\frac{n \cdot e^2 \tau}{m} \vec{E}$$

$$\vec{J} = -\sigma \vec{E}$$

# Terms to infer - microscopic

## Current Density

$$\vec{J} = \sigma \vec{E}$$

## Conductivity

$$\sigma = \frac{ne^2\tau}{m}$$

## Resistivity

$$\rho = \frac{1}{\sigma} = \frac{m}{ne^2\tau}$$



## 2.2

## OHM'S LAW

## Microscopic to macroscopic

$$J = \sigma E = \sigma \frac{V}{l}$$

$$\frac{I}{A} = \sigma \frac{V}{l}$$

$$V = I \left( \frac{l}{\sigma A} \right)$$

$R$

$$R = \frac{V}{I}$$


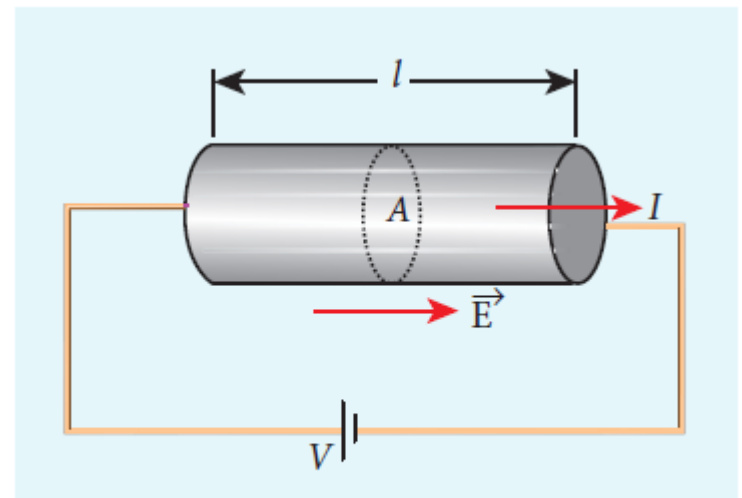
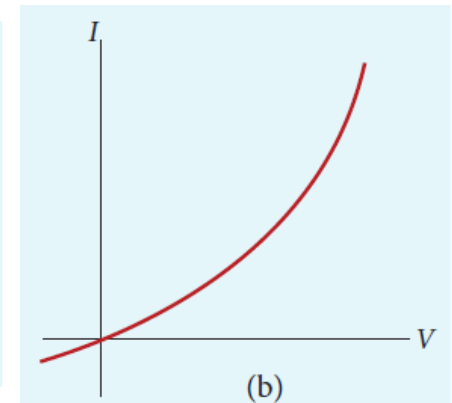


Figure 2.7 Current through the conductor

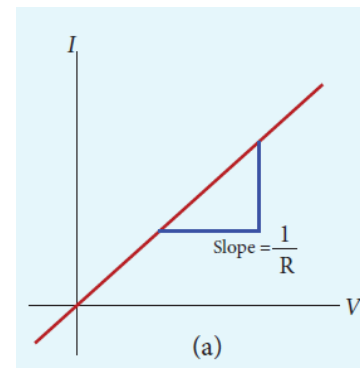

(a) Ohmic (b) Non Ohmic device

## 2.2.1 Resistivity

$$R = \frac{l}{\sigma A}$$

$$\rho = \frac{1}{\sigma}$$


$$R = \rho \frac{l}{A}$$

The resistance is the ratio of potential difference across the given conductor to the current passing through the conductor.

## **2.2.2** Resistors in series and parallel
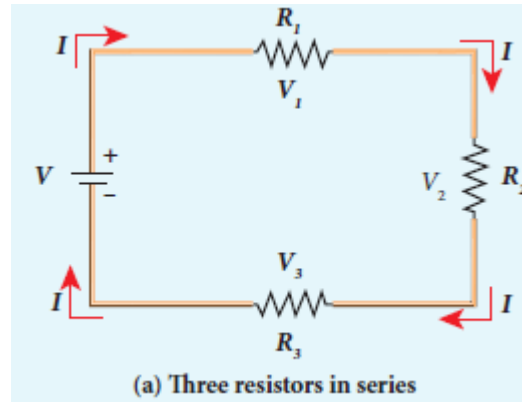
# Resistors in series

- When two or more resistors are connected end to end, they are said to be in series.
- Resistors could be simple resistors or bulbs or heating elements or other devices.




**The current  $I$  passing through all the three resistors are the same.**

$$V = V_1 + V_2 + V_3 = IR_1 + IR_2 + IR_3 \quad (2.21)$$


$$V = I(R_1 + R_2 + R_3)$$

$$V = I.R_S \quad (2.22)$$

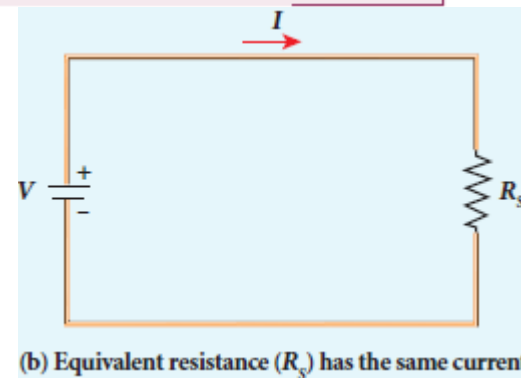**Note: The value of equivalent resistance in series connection will be greater than each individual resistance.**



# Resistors in parallel

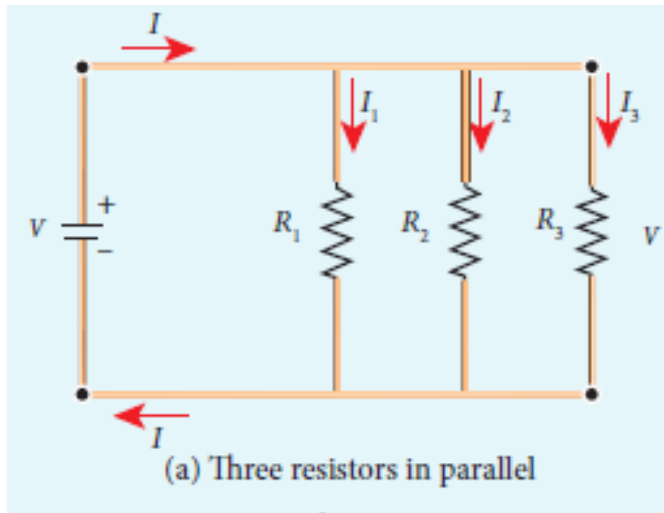

$$I = I_1 + I_2 + I_3$$


$$I_1 = \frac{V}{R_1}, I_2 = \frac{V}{R_2}, I_3 = \frac{V}{R_3}$$

$$I = \frac{V}{R_1} + \frac{V}{R_2} + \frac{V}{R_3} = V \left[ \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right]$$

$$I = \frac{V}{R_p}$$

$$\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \quad (2.26)$$

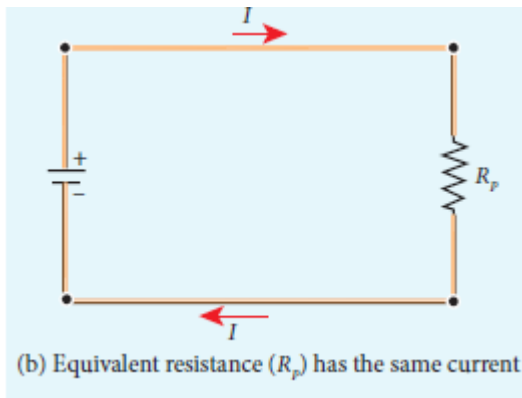
**Potential across all resistors is the same.**




Note: The value of equivalent resistance in parallel connection will be lesser than each individual resistance.

# Reducing the net work (Example 2.11)


Parallel

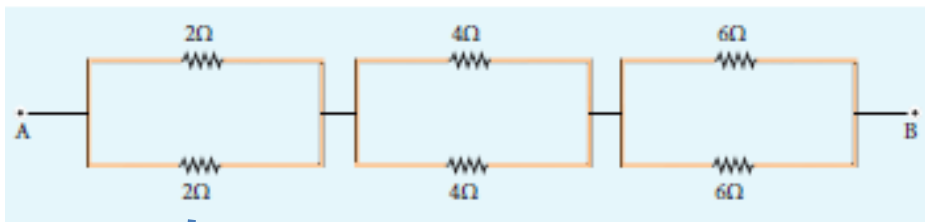



Parallel

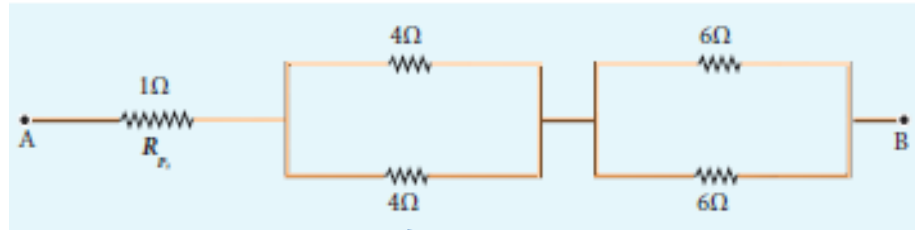


Parallel



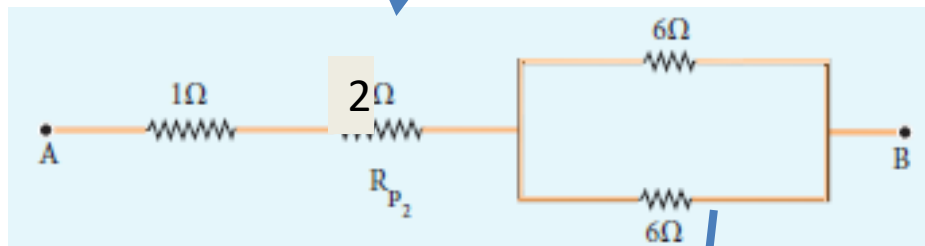


Series

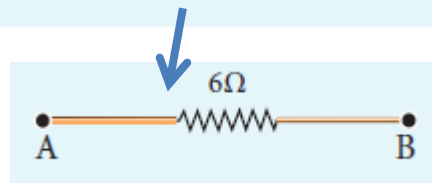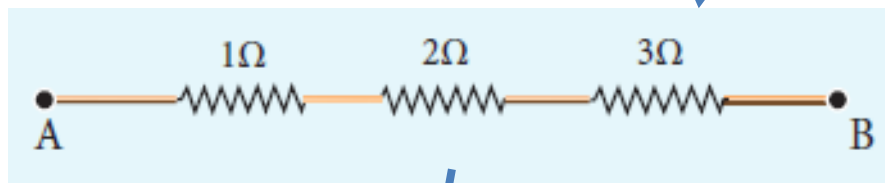

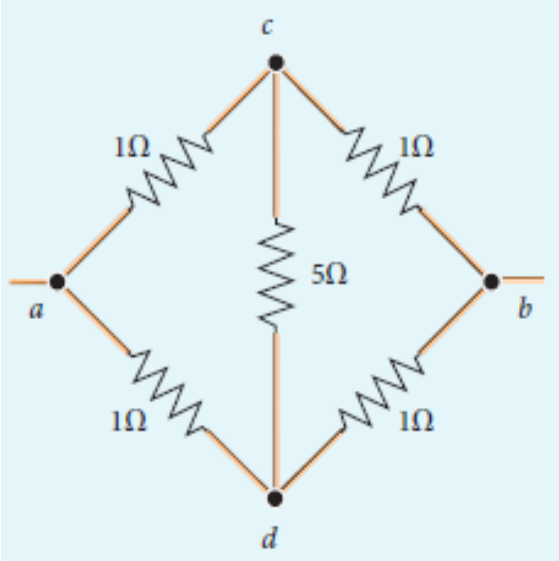

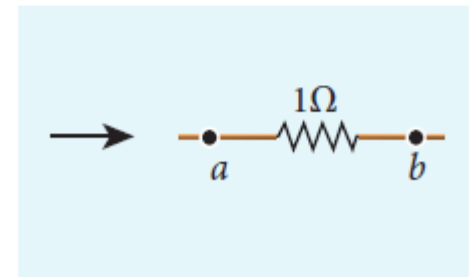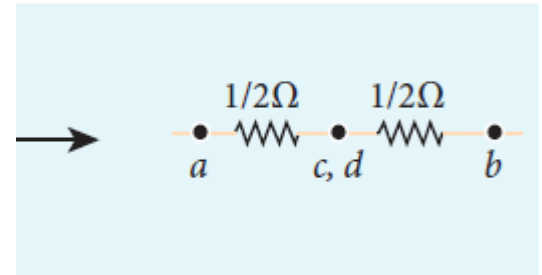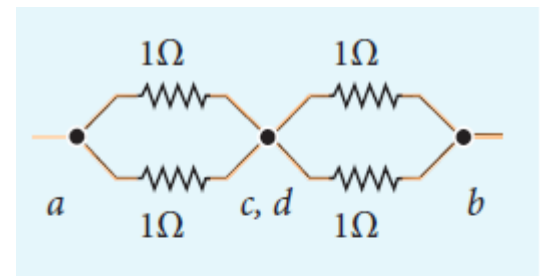- To find the equivalent resistance between the points a and b.
- we assume that current is entering the junction a.
- Since all the resistances in the outside loop are the same ( $1\Omega$ ), the current in the branches **ac** and **ad** must be equal.
- So the electric **potential at the point c and d is the same** hence no current flows into  $5\Omega$  resistance.



## 2.2.3 Color code for Carbon resistors

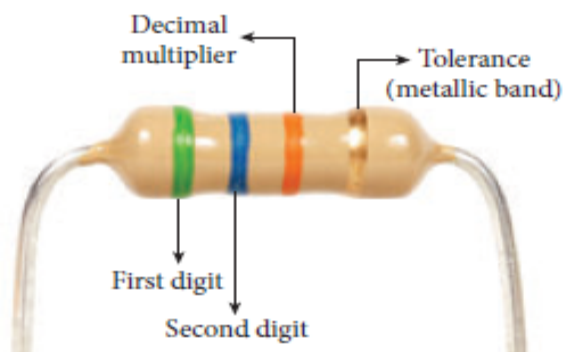


**Figure 2.11** Resistance used in our laboratory



**Note**

While reading the colour code, hold the resistor with colour bands to your left. Resistors never start with a metallic band on the left.



**Figure 2.12** Resistor color coding

**Table 2.2** Color Coding for Resistors

Color	Number	Multiplier	Tolerance
Black	0	1	
Brown	1	$10^1$	
Red	2	$10^2$	
Orange	3	$10^3$	
Yellow	4	$10^4$	
Green	5	$10^5$	
Blue	6	$10^6$	
Violet	7	$10^7$	
Gray	8	$10^8$	
White	9	$10^9$	
Gold		$10^{-1}$	5%
Sliver		$10^{-2}$	10%
Colorless			20%



## 2.2.4 Temperature dependence of resistivity


$$\rho_T = \rho_o [1 + \alpha(T - T_o)]$$

$$R_T = R_o [1 + \alpha(T - T_o)]$$


## **2.3**

# **ENERGY AND POWER IN ELECTRICAL CIRCUITS**

# ELECTRIC CELLS AND BATTERIES

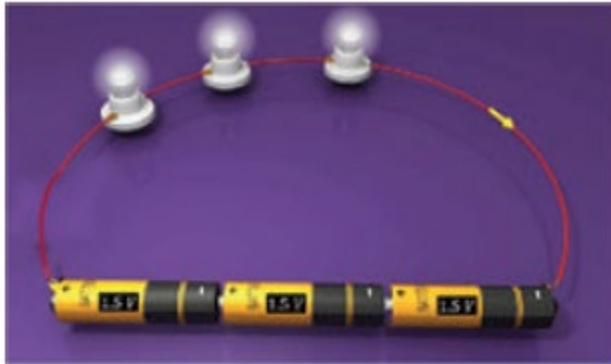


Cells in series (Schematic diagram)

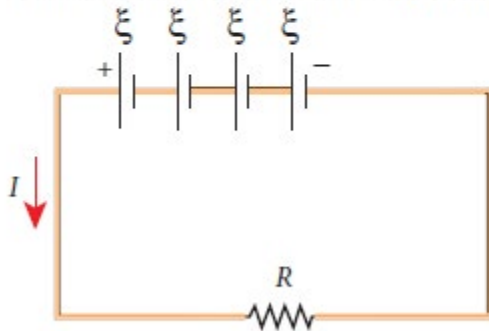

Cells in series (circuit diagram)

Figure 2.21 cells in series

**Series**

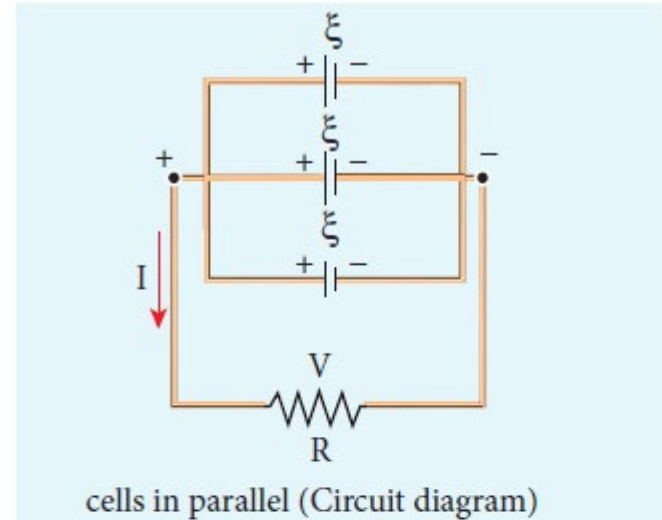


cells in parallel (Circuit diagram)



Cells in parallel (Schematic diagram)

**Parallel**
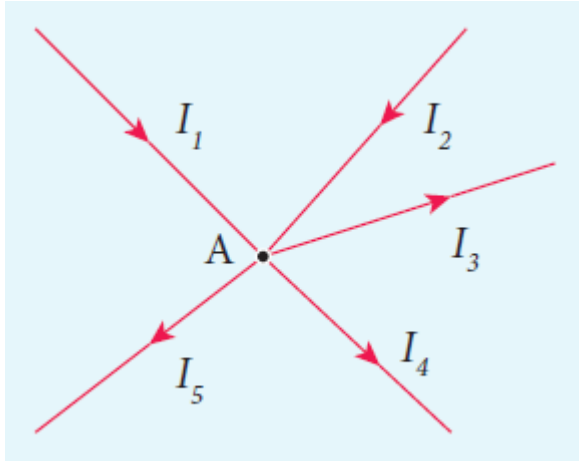
## 2.5.1 Kirchhoff's first rule (Current rule or Junction rule)



$$I_1 + I_2 - I_3 - I_4 - I_5 = 0$$

(or)

$$I_1 + I_2 = I_3 + I_4 + I_5$$


2.5.1 Kirchhoff's first rule (Current rule or Junction rule)

It states that the **algebraic sum of the currents at any junction of a circuit is zero**. It is a statement of conservation of electric charge.

## **2.5.2 Kirchhoff's Second rule (Voltage rule or Loop rule)**

**It states that in a closed circuit the algebraic sum of the products of the current and resistance of each part of the circuit is equal to the total emf included in the circuit.**

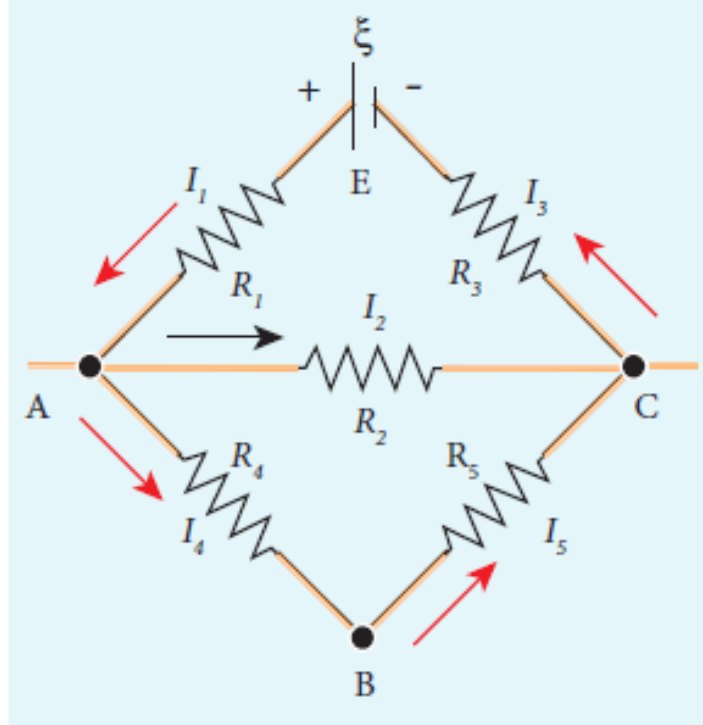**This law follows from the law of conservation of energy for an isolated system (The energy supplied by the emf sources is equal to the sum of the energy delivered to all resistors).**



Thus applying Kirchhoff's second law to the closed loop EACE

$$I_1 R_1 + I_2 R_2 + I_3 R_3 = \xi$$

and for the closed loop ABCA

$$I_4 R_4 + I_5 R_5 - I_2 R_2 = 0$$

## Application of Kirchhoff law

---

**2.5.3**    **Wheatstone's bridge**

---

**2.5.4**    **Meter bridge**

---

**2.5.5**    **Potentiometer**

## **2.6**

# **HEATING EFFECT OF ELECTRIC CURRENT**



## 2.7

### THERMOELECTRIC EFFECT

Conversion of temperature differences into electrical voltage and vice versa is known as thermoelectric effect.

# Seebeck Effect



[Thomas Johann Seebeck](#)

Seebeck discovered that in a closed circuit consisting of two dissimilar metals, when the junctions are maintained at different temperatures an emf (potential difference) is developed.

The current that flows due to the emf developed is called thermoelectric current.

The two dissimilar metals connected to form two junctions is known as thermocouple.

If the hot and cold junctions are interchanged, the direction of current also reverses. Hence the effect is reversible.

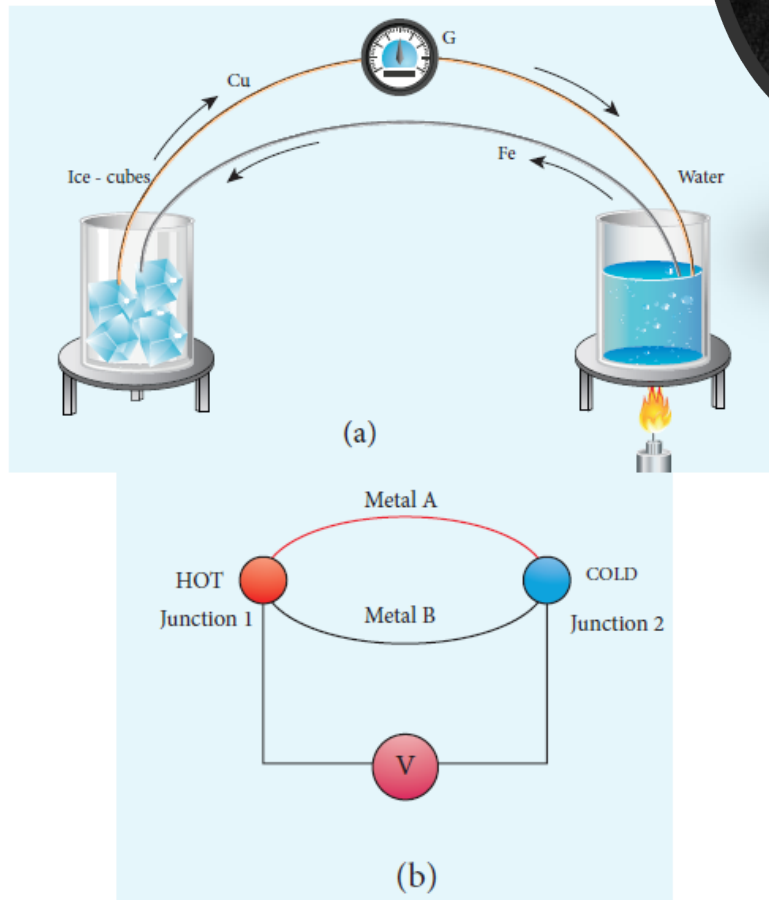


Figure 2.35 Seebeck effect (Thermocouple)

**The magnitude of the emf developed in a thermocouple depends on**

- (i) the nature of the metals forming the couple and**
- (ii) the temperature difference between the junctions.**


**Seebeck arranged the metals in a series in which any two metals can be used to construct the thermocouple.**



## 2.7.2 Peltier effect

In 1834, Peltier discovered that when an electric current is passed through a circuit of a thermocouple, heat is evolved at one junction and absorbed at the other junction.

**Peltier effect is reversible – changing the polarity (direction of current flow) changes the hot and cold junctions**

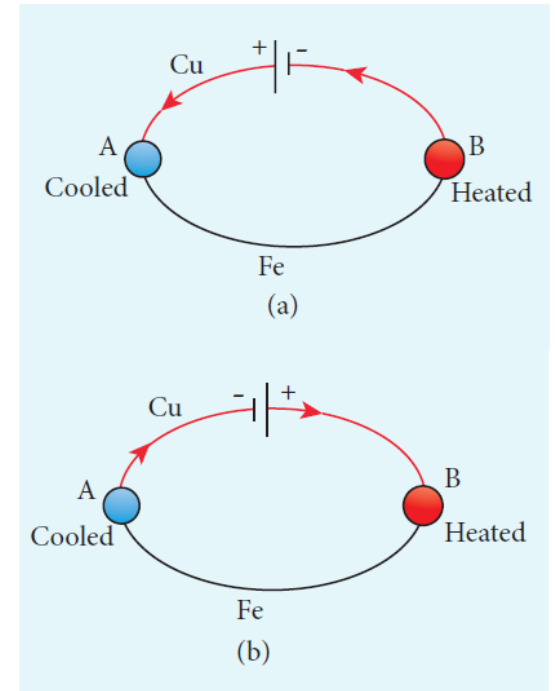


**Figure 2.36** Peltier effect: Cu – Fe thermocouple



**Peltier Thermoelectric Cooler Module**


## 2.7.3 Thomson effect

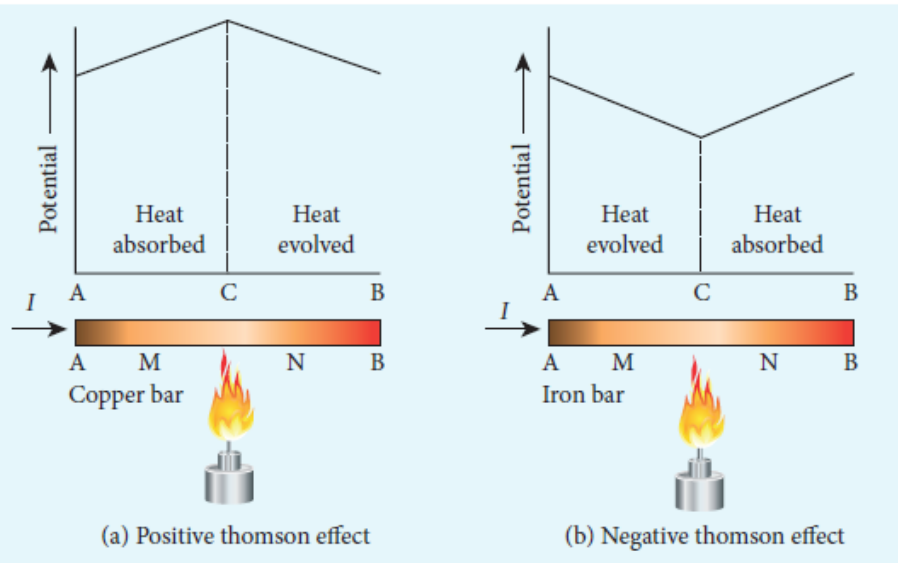

**Figure 2.37** (a) Positive Thomson effect  
(b) Negative Thomson effect

Thomson showed that if two points in a conductor are at different temperatures, the density of electrons at these points will differ and as a result the potential difference is created between these points. Thomson effect is also reversible.

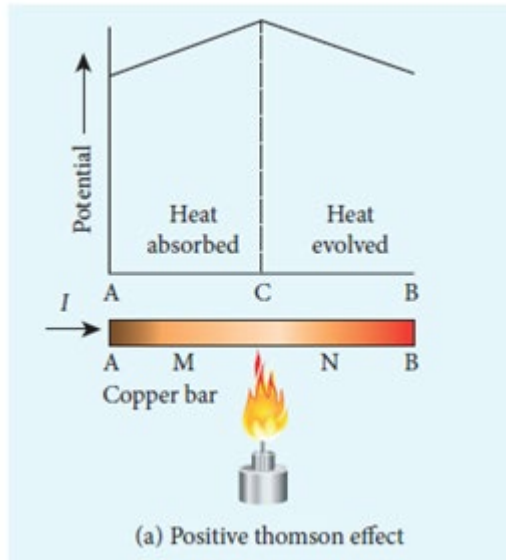**Thomson effect**, the evolution or absorption of heat when **electric current passes** through a circuit composed of a **single material** that has a **temperature difference** along its length.



**Thomson Effect is reversible**

(i) When **no current flows**, M and N at equidistant from middle point C will be at the **same temperature**.

(ii) When **current flows** (in the direction shown), **N will be at higher temperature compared to M. (B at higher temperature than A)**

(iii) From A to C heat is absorbed and C to B heat is evolved


**Positive Thomson effect.**  
Cu shows this behavior

**Negative Thomson effect.**

Fe shows this behavior

(i) When **current flows** (in the direction shown), **M will be at higher temperature compared to N. (A at higher temperature than B)**

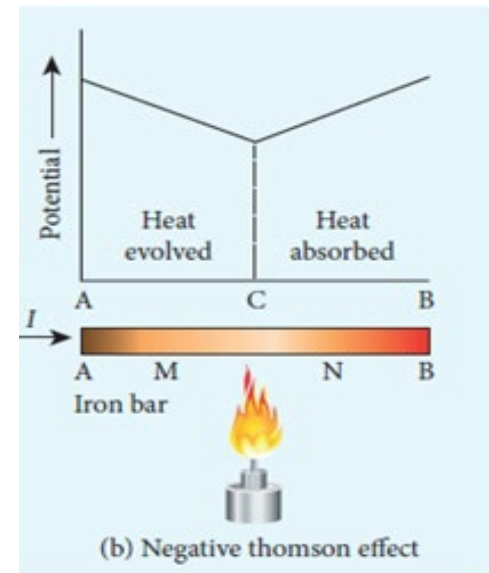(ii) From A to C heat is evolved and C to B heat is absorbed





A vibrant, close-up photograph of a large bed of petunias. The flowers are in various stages of bloom, with a mix of bright yellow and deep pink colors. The green foliage is visible between the flowers. In the center of the image, there is a white, horizontally-oriented oval with a thin red border. Inside this oval, the words "THANK YOU" are written in a bold, pink, sans-serif font. The text is slightly shadowed, giving it a 3D appearance as if it's floating above the flowers.

**THANK YOU**